

Unit 2

Sequential Logic and FSMs

EL-GY 9463: INTRODUCTION TO HARDWARE DESIGN

PROFS. SUNDEEP RANGAN, SIDDHARTH GARG

Learning Objectives


- ❑ Define **finite state machines** and identify inputs, outputs, and states
- ❑ Implement FSMs with **sequential logic** in SystemVerilog
- ❑ Break and implement functions over multiple clock cycles
- ❑ Write a **testbench** for the hardware modules
- ❑ **Simulate**, and **synthesize** the SystemVerilog using **Vivado** tools

Outline

- ➡ Registers, Clocks and Sequential Logic and Finite State Machines
 - ❑ Splitting Long Computations
 - ❑ Simulating and Synthesizing Simple Modules in Vivado

Limitations of Combinational Logic

 - ❑ No memory — cannot store past values
- ❑ Output changes immediately with input changes (no control over timing)
- ❑ Long combinational paths lead to large propagation delays
- ❑ Hard to build large systems without controlled timing boundaries
- ❑ Glitches and hazards can propagate freely
- ❑ No notion of “steps” or “cycles” — everything is continuous



Synchronous (Sequential) Logic

- ❑ Introduces **state** via **flip-flops** or **registers**
- ❑ Breaks long logic into **clocked stages**, improving performance
- ❑ Provides **predictable timing** — changes only occur on clock edges
- ❑ Makes large systems modular and easier to reason about
- ❑ Eliminates most hazards/glitches from propagating across stages
- ❑ Enables pipelining, finite-state machines, and sequential algorithms
- ❑ Allows clean interfaces between modules (valid/ready, handshakes, etc.)

Synchronous logic is the dominant paradigm for design

Clock Signal

❑ **Clock:** An alternating binary signal

- Visualized as a square wave

❑ Each period is called a **clock cycle**


- Typically, between two **rising edges**

❑ **Parameters:**

- Clock **period** T
- **Frequency** $f = \frac{1}{T}$

❑ **Typical parameters:**

 - FPGA logic: 100 to 500 MHz
- ASIC: 500 MHz to 1 GHz



Synchronous Logic Example: Counter

□ Synchronous logic:

- Updates occur on each clock cycle

□ Simple example: A down-counter

□ Potential **specification**: On clock cycle k :

- If $start[k] = 1$ and $(cnt[k] = 0)$
 $\Rightarrow cnt[k + 1] \leftarrow cnt_init[k]$
- Else $cnt[k + 1] \leftarrow \max\{0, cnt[k] - 1\}$

k	$start$	cnt_init	cnt
0	0	X	0
1	1	3	0
2	0	0	3
3	1	6	2
4	0	0	1
5	0	0	0
6	1	5	0
7	1	5	5
8	0	0	4
9	0	0	3

Key Components of a Module

❑ Counter example from previous slide:

- If $start[k] = 1$ and $(cnt[k] = 0)$
 $\Rightarrow cnt[k + 1] \leftarrow cnt_init[k]$
- Else $cnt[k + 1] \leftarrow \max\{0, cnt[k] - 1\}$

❑ Inputs: $start$ and cnt_init

- What the module takes as input

❑ Output: cnt

- What the module produces

❑ State: cnt

- What needs to be stored to compute the subsequent outputs given the inputs

What is a State?

□ **Definition:** A state is a set of variables $state[k]$ such that:


- Given $state[k]$ and inputs $input[k], input[k + 1], \dots$
- Outputs $output[k], output[k + 1], \dots$ are fully determined

□ In our case:

- $cnt[k]$ is the state
- Given $cnt[k]$ and future inputs $cnt_init[k]$ and $start[k]$
- We can fully determine future outputs $cnt[k], cnt[k + 1], cnt[k + 2], \dots$

Synchronous Logic as an FSM

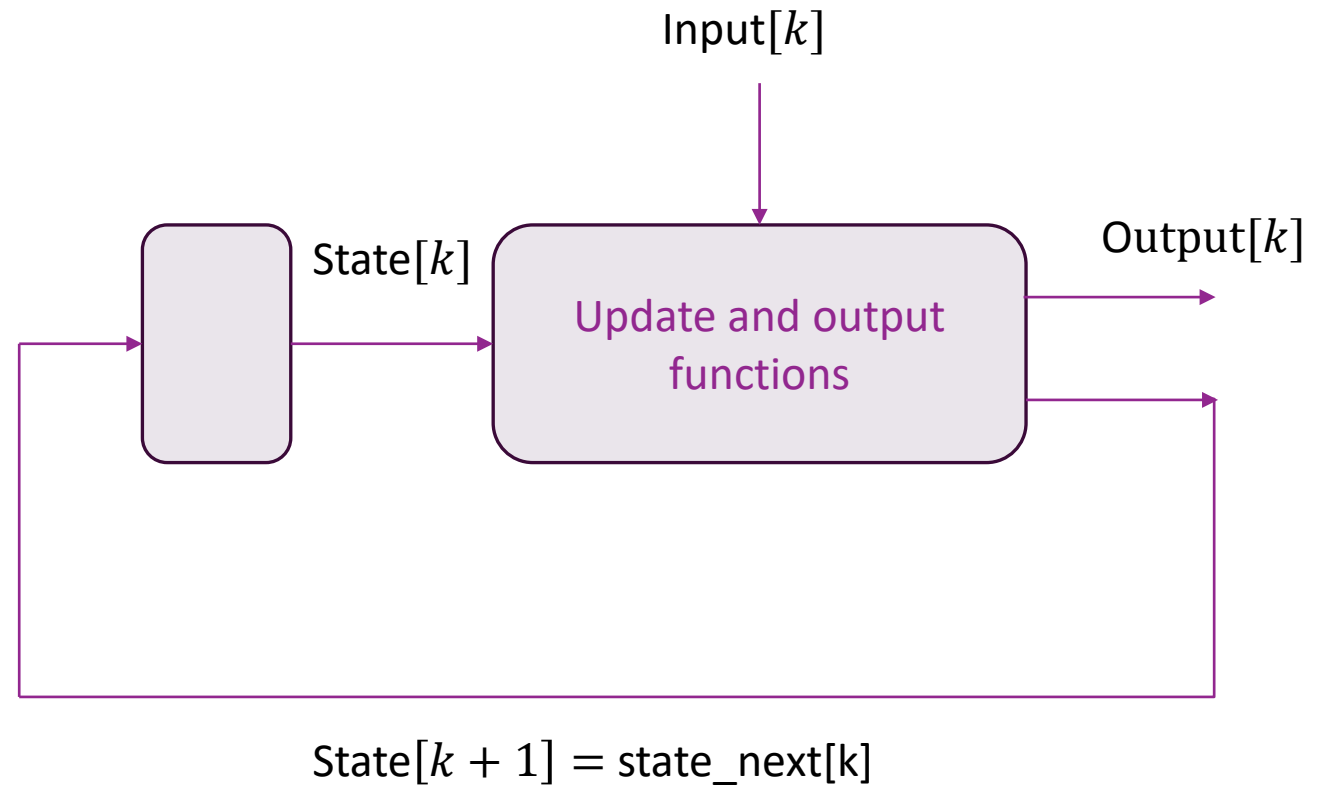- ❑ General finite state machine
- ❑ Update function:
 - $state[k + 1] = F(state[k], input[k])$
 - Describes how the state evolves
- ❑ Output function:
 - $output[k] = G(state[k], input[k])$




Building an FSM in Hardware

❑ States are stored in registers

- Basic storage element



❑ Update and output functions

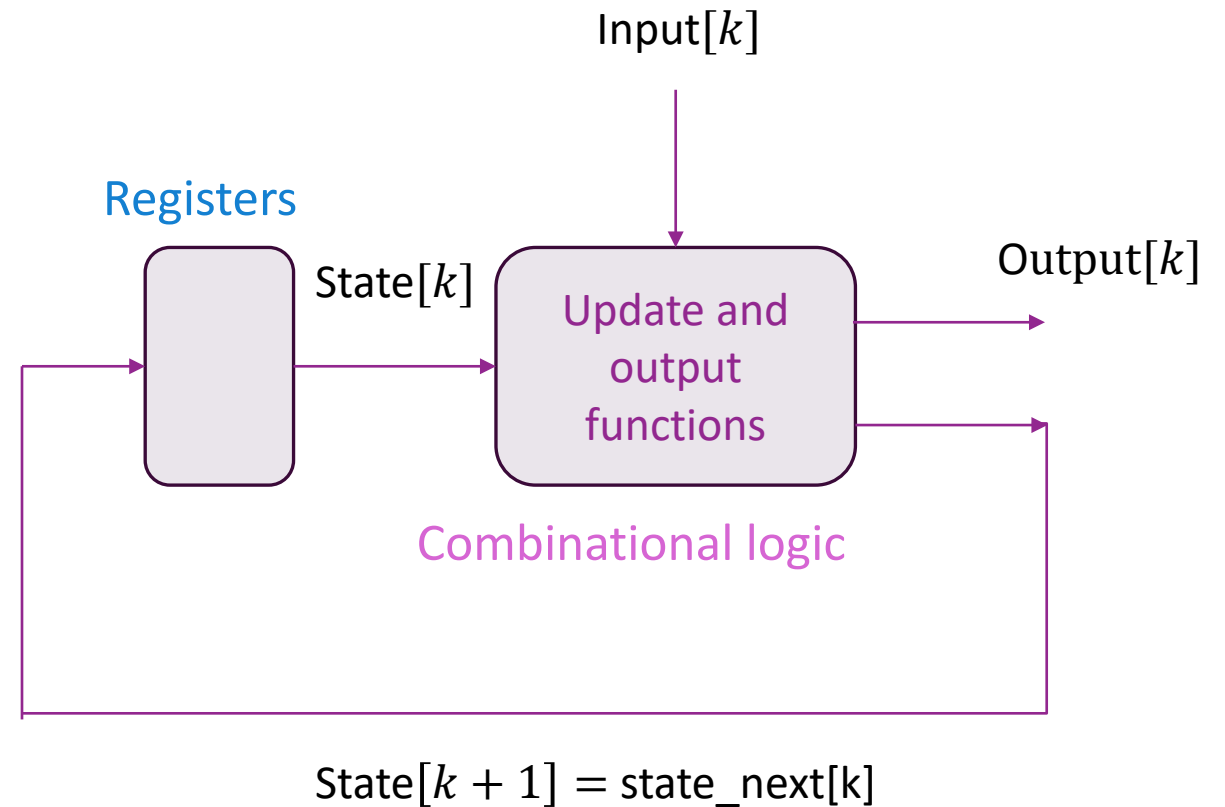- Implemented in combinational logic
- No storage
- Takes input and current state
- Produces next state and output
- Must finish within one clock cycle



Register Physical Model

  - ❑ Basic storage element in synchronous logic
- ❑ On each rising edge of clk:
 - Assigns xreg to x
- ❑ Value of xreg is maintained even if x changes
- ❑ Example below: Input is “sampled” at rising edges



Register: Discrete-Time Model


- Suppose input has value $x[k]$ in clock cycle k
- Then register output is:

$$xreg[k + 1] = x[k]$$

- A simple delay element

□ Example:

 - If $x = 4, 8, 9, 1, 2$ in clock cycles 0 to 4
- Suppose $xreg$ is initialized $xreg = 0$ in clock cycle 0
- Then $xreg = 0, 4, 8, 9, 1, 2$ in clock cycles 0 to 5



Writing the Counter in System Verilog

- ❑ The counter is a **module**
- ❑ The module definition describes:
 - Inputs and outputs
 - Must have a **clock** input
 - Typically, also a **reset**
- ❑ Does not need the internal state
 - Unless it happens to be an output

```
module counter (  
    input logic clk,  
    input logic rst,  
    input logic start,  
    input logic [3:0] cnt_init,  
    output logic [3:0] cnt  
);
```

Counter Main Body

Combinational block (always_comb)

- Takes current state and input
- Describes next state and output

```
);  
logic [3:0] cnt_next;  
always_comb begin  
    cnt_next = cnt;  
    if ((start) && (cnt == 0)) begin  
        cnt_next = cnt_init;  
    end else if (cnt > 0) begin  
        cnt_next = cnt - 1;  
    end else begin  
        cnt_next = 0;  
    end  
end
```

always_ff

- Registers values for next state

```
always_ff @(posedge clk) begin  
    if (rst) begin  
        cnt <= 0;  
    end else begin  
        cnt <= cnt_next;  
    end  
end
```

Putting it Together

- ❑ We now have the FSM description
- ❑ Three parts
- ❑ Module declaration
 - Inputs, outputs
- ❑ Always_comb block
 - Describes next state
- ❑ Always_ff block
 - Updates state from next_state

```
module counter (  
    input logic clk,  
    input logic rst,  
    input logic start,  
    input logic [3:0] cnt_init,  
    output logic [3:0] cnt  
);  
    logic [3:0] cnt_next;  
    always_comb begin  
        cnt_next = cnt;  
        if ((start) && (cnt == 0)) begin  
            cnt_next = cnt_init;  
        end else if (cnt > 0) begin  
            cnt_next = cnt - 1;  
        end else begin  
            cnt_next = 0;  
        end  
    end  
    always_ff @(posedge clk) begin  
        if (rst) begin  
            cnt <= 0;  
        end else begin  
            cnt <= cnt_next;  
        end  
    end  
endmodule
```


Blocking vs. Non-Blocking

❑ Blocking assignment

- Use = in SV
- Performed sequentially
- Assigns temporary (i.e., non-state variables)
- Used in always_comb or always_ff block

❑ Non-blocking assignment

- Use <= in SV
- Assigns registers / states
- Only in always_ff block
- Always update in parallel

```
);  
logic [3:0] cnt_next;  
always_comb begin  
    cnt_next = cnt;  
    if ((start) && (cnt == 0)) begin  
        cnt_next = cnt_init;  
    end else if (cnt > 0) begin  
        cnt_next = cnt - 1;  
    end else begin  
        cnt_next = 0;  
    end  
end
```

```
always_ff @(posedge clk) begin  
    if (rst) begin  
        cnt <= 0;  
    end else begin  
        cnt <= cnt_next;  
    end  
end
```

Example Problem

Sequential updates: Consider the following SystemVerilog code:

```
always_ff @(posedge clk) begin
    x <= x + v;
    if (x > 30) begin
        v <= -10;
    end else if (x < 0) begin
        v <= 10;
    end
end
```

Starting from $(x, v) = (15, 10)$, what are the values of (x, v) for the next 5 clock cycles?

Try Answer on LLM Auto-Grader

- ☐ Use AI to get instant feedback
- ☐ Enter your answer
- ☐ Hit Grade

Your Solution


Grade

Part

All ▾

Model: gpt-4.1-mini ▾

Timeout (s): 20

 **NYU** OpenAI Grader for NYU Applied Hardware Design
Profs. Sundeep Rangan, Siddharth Garg

Instructions for using this grader

Init: unit1_basic_logic ▾ Save Results Load Results

Question: Sequential updates ▾

Student File: Choose File No file chosen Load

Question

Sequential updates:
Consider the following SystemVerilog code:

```
always_ff @(posedge clk) begin
    x <= x + v;
    if (x > 30) begin
        v <= -10;
    end else if (x < 0) begin
        v <= 10;
    end
end
end
```

Solution: FSM Model

- ❑ Write the **FSM model**
- ❑ Remember: Updates in `always_ff` are in parallel
 - Test $x > 30$ is based on **current** cycle value, not next cycle

k	$x[k]$	$v[k]$
0	15	10
1	25	10
2	35	10
3	45	-10
4	35	-10
5	25	-10

```
always_ff @(posedge clk) begin
    x <= x + v;
    if (x > 30) begin
        v <= -10;
    end else if (x < 0) begin
        v <= 10;
    end
end
```



Equivalent FSM model

$$x[k + 1] = x[k] + v[k]$$

if $x[k] > 30$
 $v[k + 1] = -10$
else if $(x[k] < 0)$
 $v[k + 1] = 10$
 $v[k + 1] = v[k]$

In-Class Exercise

5. *Bouncing ball*: We simulate a ball moving in one-dimensional space between two walls at positions 0 and 100. The ball has a position x and a velocity v . At each time step, the ball first moves according to its velocity:

$$x \leftarrow x + v.$$

If this motion causes the ball to go past a wall, the ball “bounces” and reverses direction. The bounce should behave the same way a real ball would: the ball cannot pass through the wall, and the rebound distance should be consistent with how far it would have travelled past the wall.


For example:

- If $(x, v) = (40, 10)$, then the ball moves to 50, which is inside the interval, so the next state is $(50, 10)$.
- If $(x, v) = (96, 10)$, then the ball would move to 106, which is past the right wall at 100. After bouncing, the ball ends up at position 94 with velocity -10 .
- If $(x, v) = (3, -10)$, then the ball would move to -7 , which is past the left wall at 0. After bouncing, the ball ends up at position 7 with velocity 10.

Write the SystemVerilog code for the updates for x and v . You do not need to include the module declaration, just the `always_ff` and `always_comb` blocks.



In-Class Exercise

 

Instructions for using this grader

Unit:

Question:

Student File: No file chosen

Question

Bouncing ball:
We simulate a ball moving in one-dimensional space between two walls at positions 0 and 100. The ball has a position x and a velocity v .
At each time step, the ball first moves according to its velocity:
 $x \leftarrow x + v$.
If this motion causes the ball to go past a wall, the ball "bounces" and reverses direction. The bounce should behave the same way a real ball would: the ball cannot pass through the wall, and the rebound distance should be consistent with how far it would have travelled past the wall.

For example:
- If $(x,v) = (40,10)$, then the ball moves to 50, which is inside the

☐ Try answering on the auto-grader



Outline

☐ Registers, Clocks and Sequential Logic and Finite State Machines

 ☐ Splitting Long Computations

☐ Simulating and Synthesizing Simple Modules in Vivado

Synchronous Version of ReLU + Linear

- Recall early combinational example

$$y = \max\{ax + b, 0\}$$

- A potential synchronous version could work as follows


- On each clock cycle:

- Register input x to a state $xreg$

- Output $y[k]$ combinatorially from $xreg[k]$

- Why?

 - Output computation has a full clock cycle
 - Output is in a known state by the end of each clock cycle



Synchronous Module Declaration

❑ Making module synchronous is easy

❑ First add two inputs to ports

- Clock signal
- Reset

```
module relu_lin (  
    input logic clk,           ← Clock  
    input logic rst,          ← Reset  
    input logic signed [31:0] x,  
    input logic signed [31:0] a,  
    input logic signed [31:0] b,  
    output logic signed [31:0] y  
);
```

System Verilog Main Body

□ Synchronous logic has two parts

□ `always_ff`:

- Assigns register outputs
- All operations are in parallel (non-blocking)
- Our example: Saves inputs to registers

□ `always_comb`:

- Assigns signals via combinational logic
- Operations are sequential (blocking)
- Our example: Computes output from registered inputs

```
logic signed [31:0] x_reg, a_reg, b_reg;
```

```
always_comb begin
```

```
    logic signed [31:0] mult_out, add_out;
```

```
    mult_out = x_reg * a_reg;
```

```
    add_out = mult_out + b_reg;
```

```
    y = (add_out > 0) ? add_out : 0;
```

```
end
```

```
always_ff @(posedge clk) begin
```

```
    if (rst) begin
```

```
        x_reg <= 0;
```

```
        a_reg <= 0;
```

```
        b_reg <= 0;
```

```
    end else begin
```

```
        x_reg <= x;
```

```
        a_reg <= a;
```


```
        b_reg <= b;
```

```
    end
```

```
end
```

Synchronous Block Diagram

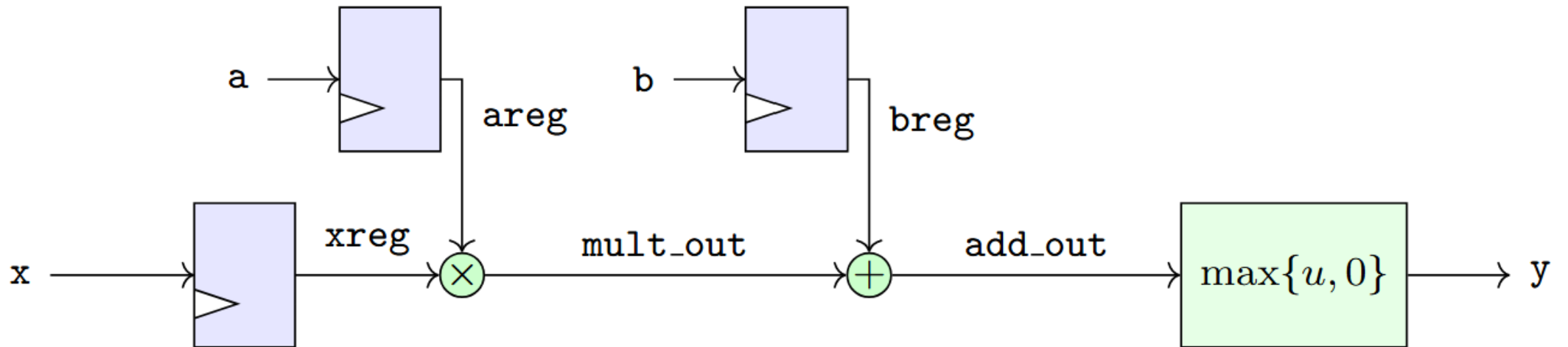- ❑ Inputs are registered
- ❑ Output is combinational from input



FSM Description

States:

- $x_{reg}[k], a_{reg}[k], b_{reg}[k]$

Combinational statements:

- $mult_out[k] = x_{reg}[k] * a_{reg}[k]$
- $add_out[k] = x_{reg}[k] * a_{reg}[k] + b_{reg}[k]$
- $y[k] = \max\{0, x_{reg}[k] * a_{reg}[k] + b_{reg}[k]\}$

State updates:

- $x_{reg}[k + 1] = x[k], a_{reg}[k + 1] = a[k], \dots$

Putting it together:

$$y[k + 1] = \max\{0, a[k]x[k] + b[k]\}$$

- Desired output with one cycle delay

```
logic signed [31:0] x_reg, a_reg, b_reg;
```

```
always_comb begin
```

```
    logic signed [31:0] mult_out, add_out;
```

```
    mult_out = x_reg * a_reg;
```

```
    add_out = mult_out + b_reg;
```

```
    y = (add_out > 0) ? add_out : 0;
```

```
end
```

```
always_ff @(posedge clk) begin
```

```
    if (rst) begin
```

```
        x_reg <= 0;
```

```
        a_reg <= 0;
```

```
        b_reg <= 0;
```

```
    end else begin
```

```
        x_reg <= x;
```

```
        a_reg <= a;
```


```
        b_reg <= b;
```

```
    end
```

```
end
```

A More Complex Example

 
- ❑ Consider a quadratic function: $y = w_2x^2 + w_1x + w_0$
- ❑ For simplicity, assume w_0, w_1, w_2 are fixed parameters
- ❑ Single cycle implementation to the right



```
module quad_func #(
    parameter int w2 = 0,
    parameter int w1 = 0,
    parameter int w0 = 0
) (
    input logic clk,
    input logic int x,
    output logic int y
);
    int xreg;
    always_ff @(posedge clk) begin
        xreg <= x;
    end
    always_comb begin
        logic int xsq, xsq_w2, x_w1;
        xsq = xreg * xreg;
        xsq_w2 = w2 * xsq;
        x_w1 = w1 * xreg;
        y = xsq_w2 + x_w1 + w0;
    end
end
```

 Problems with Single Cycle Implementation

- ❑ Problem: Each clock cycle has a “lot” to do
- ❑ Longest path from $x_reg \rightarrow y$ has:
 - Compute xsq : One multiply
 - Compute xsq_w2 : One multiply
 - Add $w0$: One addition
 - We will discuss finding longest paths in detail later
- ❑ In general, two multiplications in one clock cycle is hard
- ❑ Typically, we limit to one multiplication
 - More on this later




```
always_comb begin
    logic int xsq, xsq_w2, x_w1;
    xsq = xreg * xreg;
    xsq_w2 = w2 * xsq;
    x_w1 = w1 * xreg;
    y = xsq_w2 + x_w1 + w0;
end
```

A Two Cycle Design

❑ We can reduce the computation per cycle by breaking operation in two cycles

❑ Register two intermediate terms:

 - $xsq = xreg * xreg$
- $lin_term = w1 * xreg + w0$



```
int xreg;
always_ff @(posedge clk) begin
    xsq <= xreg * xreg;
    lin_term <= w1 * xreg + w0;
    xreg <= x;
end
always_comb begin
    y = w2*xsq + lin_term;
end
```

Analysis

❑ Registers:

- $xsq[k], lin_term[k], xreg[k]$

❑ Updates:

- $y[k] = w2 * xsq[k] + lin_term[k]$
- $xsq[k + 1] = xreg[k]^2$
- $lin_term[k + 1] = w1 * xreg[k] + w0$

❑ Substituting in values:

- $y[k] = w2 * xreg[k - 1]^2 + w1 * xreg[k - 1] + w0$
- $y[k] = w2 * x[k - 2]^2 + w1 * x[k - 2] + w0$

❑ So, output matches desired equation

- But at a two cycle delay

```
int xreg;
always_ff @(posedge clk) begin
    xsq <= xreg * xreg;
    lin_term <= w1 * xreg + w0;
    xreg <= x;
end
always_comb begin
    y = w2*xsq + lin_term;
end
```


In Class Problem

ReLU function: We wish to implement the function:

$$y = ax^2 + \max\{bx, 0\} + c,$$

for an input x and constants a , b , and c .

Write the SystemVerilog code to implement this function over two clock cycles. Specifically, the input x should be registered in the first clock cycle, and the output y should be produced in the second clock cycle. Make sure that no clock cycle requires two or more multiplications that cannot be parallelized.

□ Hint:

- Write the computation graph for $x \rightarrow y$
- Add registers at input and intermediate variables

Instructions for using this grader

Unit:

Question:

Student File: No file chosen

Question

ReLU function: We wish to implement the function:

$$y = a x^2 + \max\{ b x, 0 \} + c,$$

for an input x and constants a , b , and c .

Write the SystemVerilog code to implement this function over two clock cycles.


Outline

❑ Registers, Clocks and Sequential Logic and Finite State Machines

❑ Splitting Long Computations

 Simulating and Synthesizing Simple Modules in Vivado

Building the Hardware Roadmap

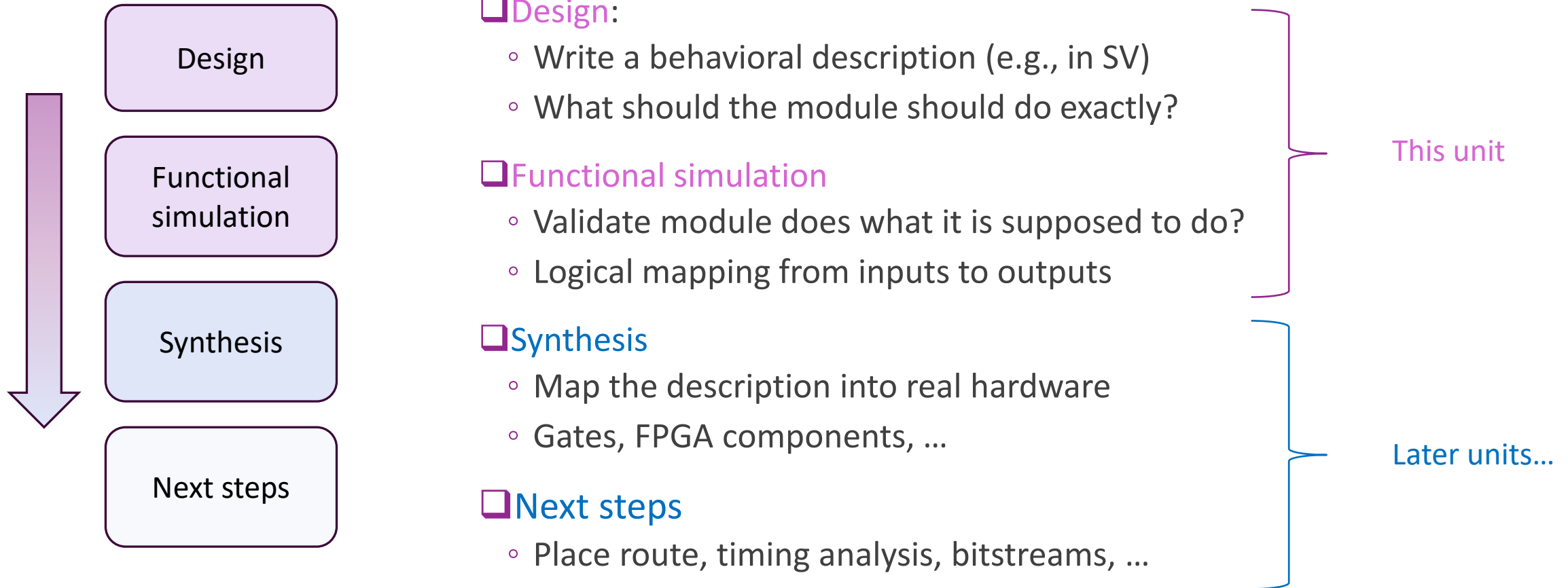

Linear+ReLU Example

- ❑ All files in github repo:
hwdesign/demos/fsm
- ❑ Define counter in file counter.sv

```
module lin_relu #(
    parameter WIDTH = 16
)(
    input logic          clk,
    input logic          rst,    // sync
    input logic signed [WIDTH-1:0] w_in,
    input logic signed [WIDTH-1:0] b_in,
    input logic signed [WIDTH-1:0] x_in,
    output logic signed [WIDTH-1:0] y_out
);
```

```
// Registered inputs
logic signed [WIDTH-1:0] w_reg, b_reg, x_reg;

// Intermediate value
logic signed [WIDTH-1:0] u;


// Register the inputs
always_ff @(posedge clk) begin
    if (rst) begin
        w_reg <= '0;
        b_reg <= '0;
        x_reg <= '0;
    end else begin
        w_reg <= w_in;
        b_reg <= b_in;
        x_reg <= x_in;
    end
end

// Combinational output
always_comb begin
    u = w_reg * x_reg + b_reg;
    y_out = (u > 0) ? u : 0;
end
```

Next Step: Build a Testbench


□ Testbench

 - A second SV module
- Connects to device under test (i.e, module we want to test)
- TB provides DUT inputs
- TB verifies DUT outputs are correct



Testbenches are not Synthesized

 - ❑ Testbenches are for simulation only
- ❑ They will not be synthesized
- ❑ Can include **un-synthesizable** constructs
 - Print statements
 - File read and write
 - Complex data structures
- ❑ Modern trend:
 - Write TB in higher level language
 - E.g., python



Testbench Declaration

❑ Testbench: a module to test the module

- Will not be synthesized
- Can have un-synthesizable constructs
- Ex: Read / write from file

```
module tb_lin_relu;

    localparam WIDTH = 16;
    localparam time CLK_PERIOD = 10ns;

    logic clk = 0;
    logic rst = 1;
    logic signed [WIDTH-1:0] x_in;
    logic signed [WIDTH-1:0] w_in;
    logic signed [WIDTH-1:0] b_in;
    logic signed [WIDTH-1:0] y_out;
```

❑ Create a clock

```
// Clock generation
always #(CLK_PERIOD/2) clk = ~clk;
```

❑ Instantiate an instance of module to test

- Called the DUT = device under test
- Connect DUT to testbench signals

```
// Instantiate DUT
lin_relu #(
    .WIDTH(WIDTH)
) dut (
    .clk(clk),
    .rst(rst),
    .w_in(w_in),
    .b_in(b_in),
    .x_in(x_in),
    .y_out(y_out)
);
```

Test Vectors

- ❑ Create a set of test inputs
- ❑ Loop through inputs
- ❑ Put one new input each clock cycle
- ❑ Testbench uses an initial construct
 - Enables sequential set of events

```
// Define test vectors
test_vector_t test_vectors[] = '{
    '{x: 10, w: 3, b: 15},
    '{x: -4, w: 10, b: 4},
    '{x: 8, w: 12, b: -5}
};
```

```
for (int i = 0; i < test_vectors.size(); i++) begin

    #(0.1*CLK_PERIOD) // hold time before changing input
    x_in = 'x; // initial indeterminate value
    w_in = 'x;
    b_in = 'x;
    #(0.15*CLK_PERIOD); // Small delay for propagation time
    x_in = test_vectors[i].x;
    w_in = test_vectors[i].w;
    b_in = test_vectors[i].b;

    // Clock cycle
    @(posedge clk);

    // Compute expected value for verification (optional)
    x = test_vectors[i].x;
    w = test_vectors[i].w;
    b = test_vectors[i].b;
    y_exp = (w * x + b > 0) ? (w * x + b) : 0;

    $display("Test %0d: x_in=%0d, y_out=%0d, y_exp=%0d",
            i, x, y_out, y_exp);

end
```


Initial Block

- ❑ Runs once at time 0 of the simulation
 - (or at its scheduled start time if delayed).
- ❑ Statements inside run sequentially
 - like a small program.
- ❑ Not synthesizable for hardware
 - Simulation-only construct.
 - Used for test benches
- ❑ Concurrency:
 - initial blocks and always blocks.

```
initial begin
    // Define test vectors
    test_vector_t test_vectors[] = '{
        '{x: 10, w: 3, b: 15},
        '{x: -4, w: 10, b: 4},
        '{x: 8, w: 12, b: -5}
    };

    // Local temporaries for expected value computation
    logic signed [WIDTH-1:0] x;
    logic signed [WIDTH-1:0] w;
    logic signed [WIDTH-1:0] b;
    logic signed [WIDTH-1:0] y_exp;

    // Reset for a few cycles
    repeat (1) @(posedge clk);
    rst = 0;

    for (int i = 0; i < test_vectors.size(); i++) begin

        #(0.1*CLK_PERIOD) // hold time before changing inp
        x_in = 'x; // initial intedeterminate value
        w_in = 'x;
        b_in = 'x;
        #(0.15*CLK_PERIOD); // Small delay for propagatio
```

Test Results

- ❑ Test results outputs
- ❑ Match expected values

```
Test 0: x_in=10, y_out=45, y_exp=45  
Test 1: x_in=-4, y_out=0, y_exp=0  
Test 2: x_in=8, y_out=91, y_exp=91
```